

Figure 1: 1-bit full adder

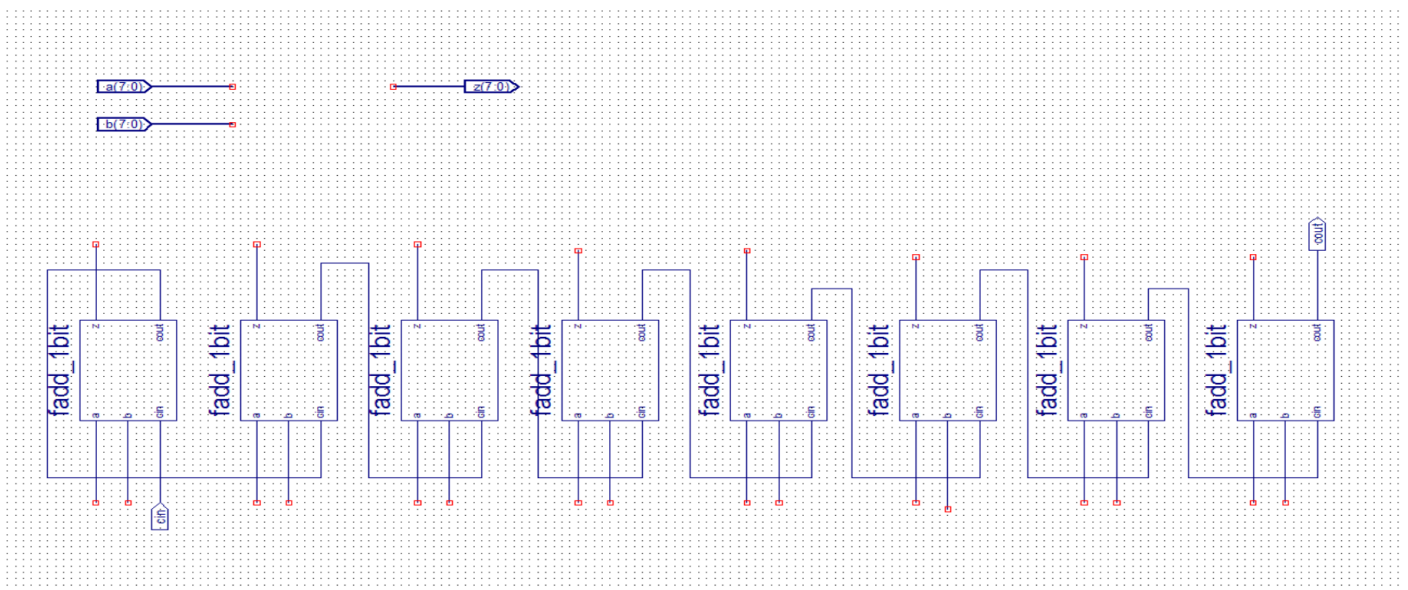


Figure 2: 8-bit full adder

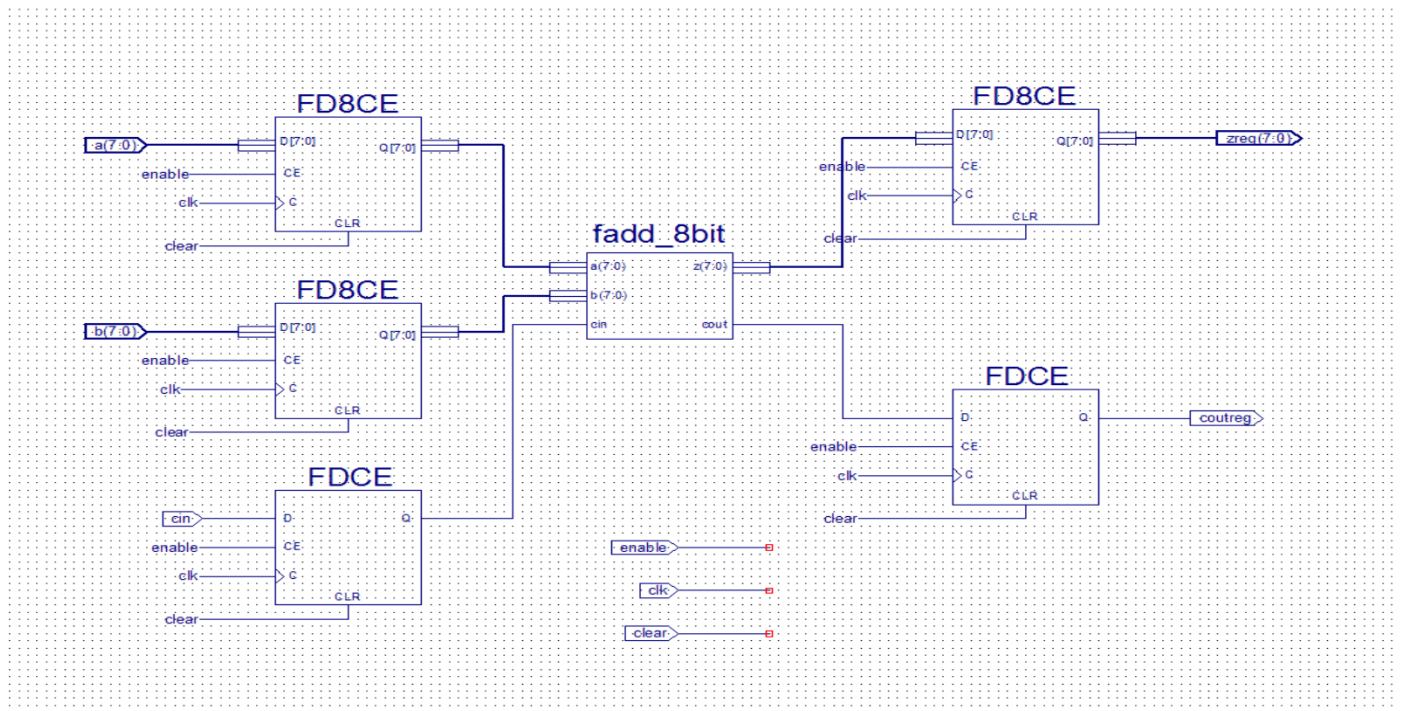


Figure 3: 8-bit full adder with DFFs

 


Figure 4: waveform of 8-bit full adder with DFFs

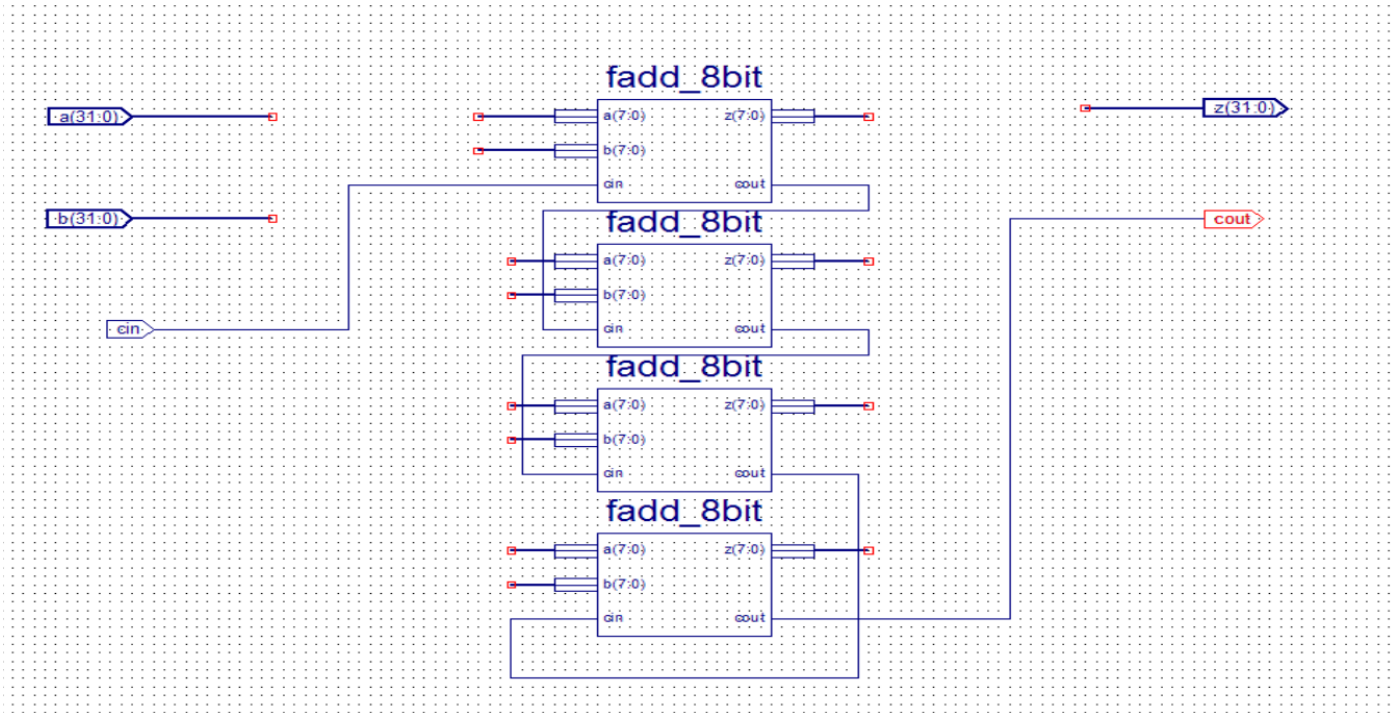


Figure 5: 32-bit full adder

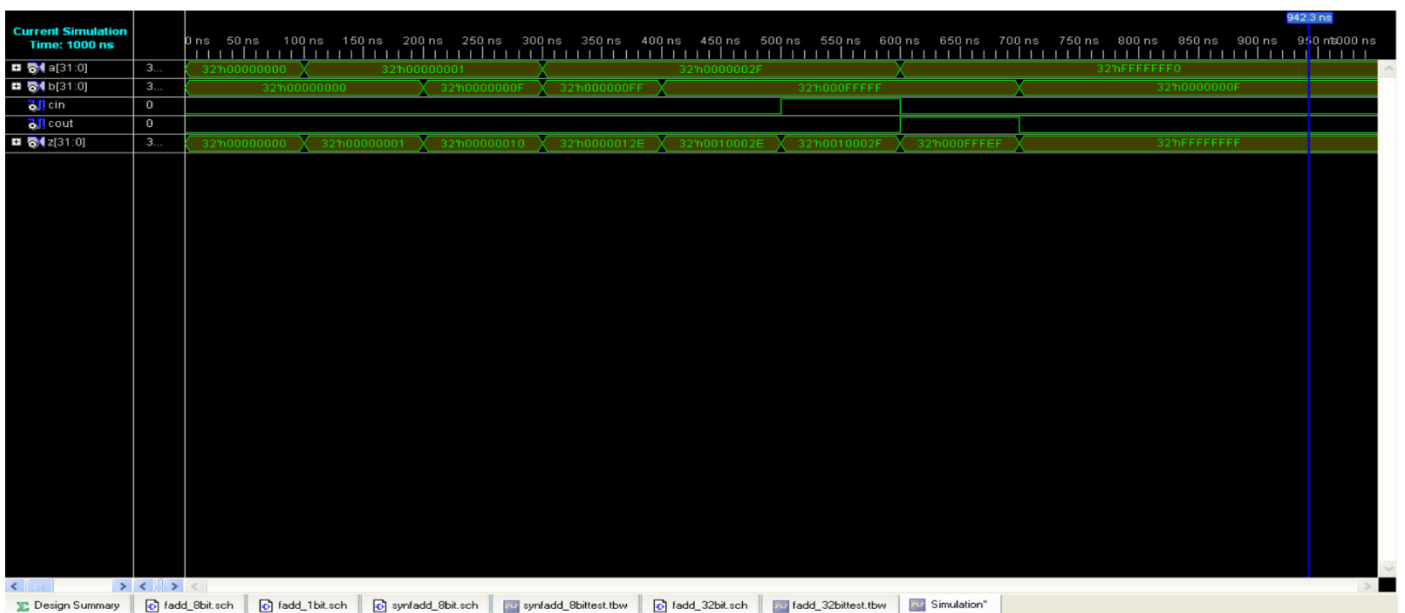


Figure 6: waveform of 32-bit full adder

32-bit ALU (schematic):

Functions:

1. 32-bit adder, when $\text{opr}(2:0) == 000$;
2. 32-bit subtractor, when $\text{opr}(2:0) == 001$;
3. 32-bit logical shifter, $\text{shiftdir} == 0$ is left shift, $\text{shiftdir} == 1$ is right shift, every time shifts 1 bit, $\text{opr}(2:0) == 010$;
4. 32-bit and, $\text{opr}(2:0) == 011$;
5. 32-bit or, when $\text{opr}(2:0) == 1XX$;

 


Figure 7: 8-bit xor

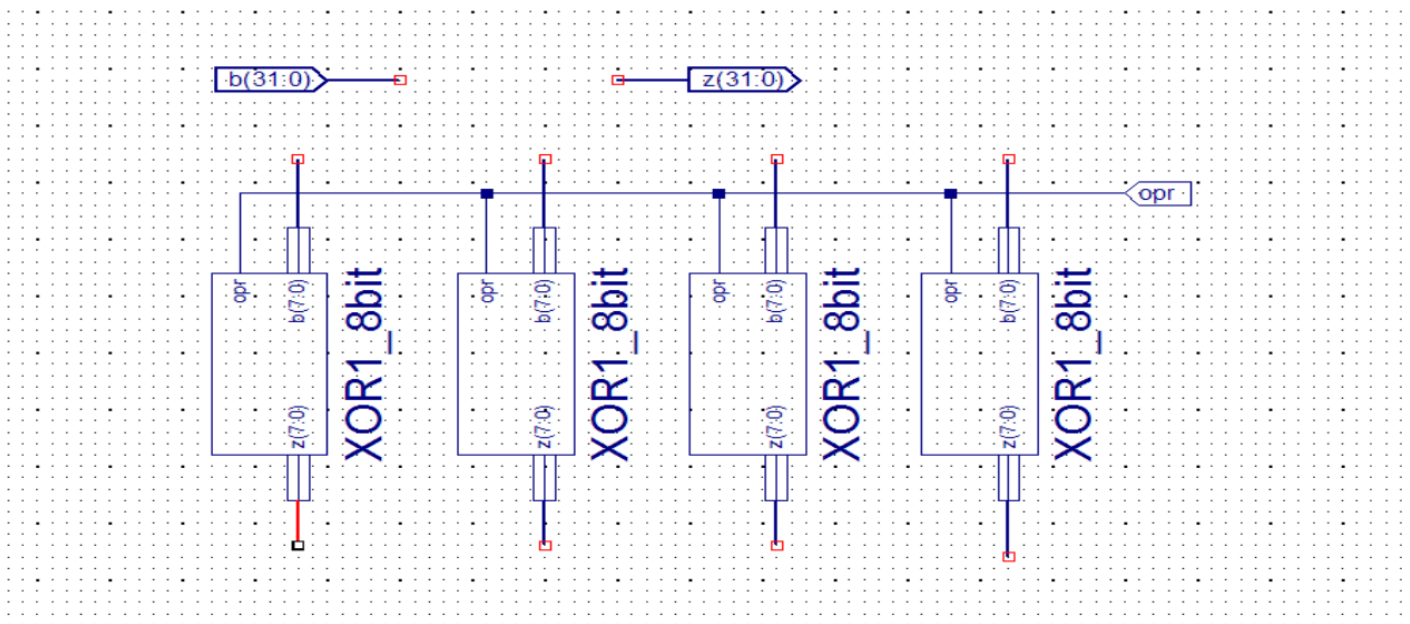


Figure 8: 32-bit xor

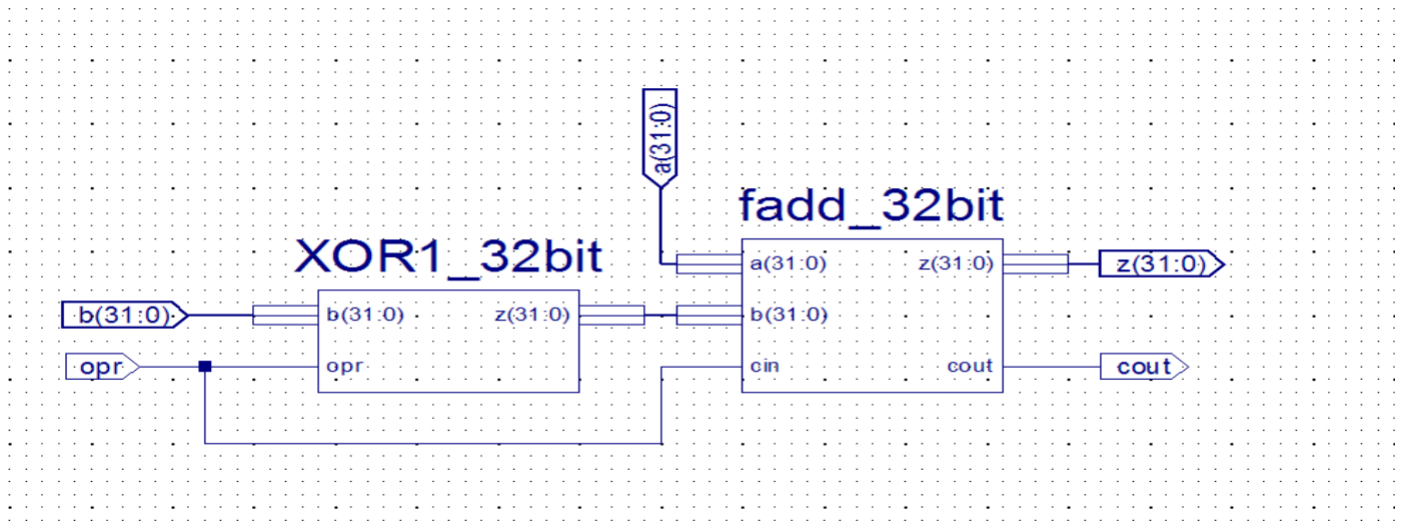


Figure 9: 32-bit subtractor

 


Figure 10: waveform of 32-bit subtractor

 


Figure 11: 1-bit 2-to-1 mux

 


Figure 12: 32-bit logical shifter

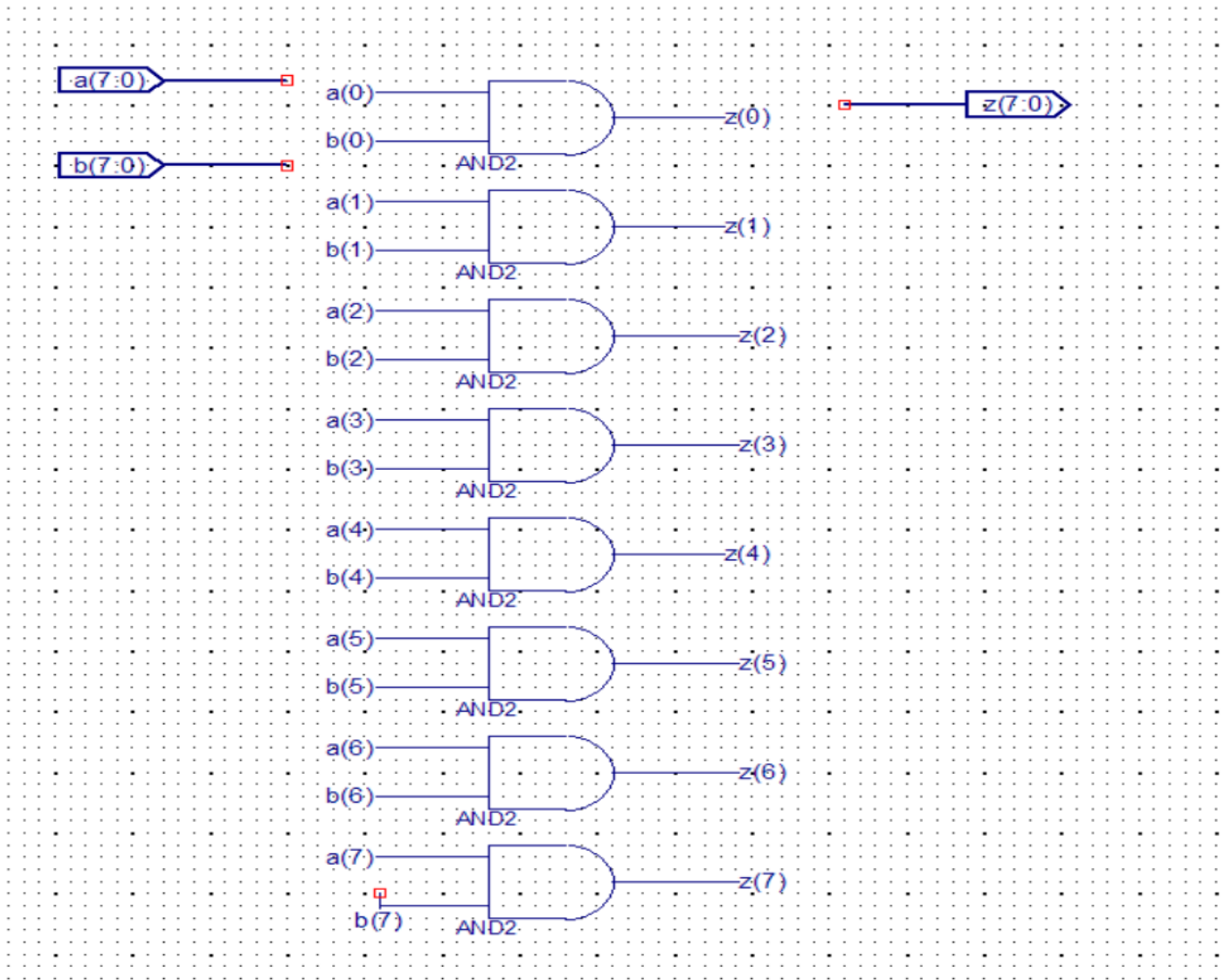


Figure 13: 8-bit and

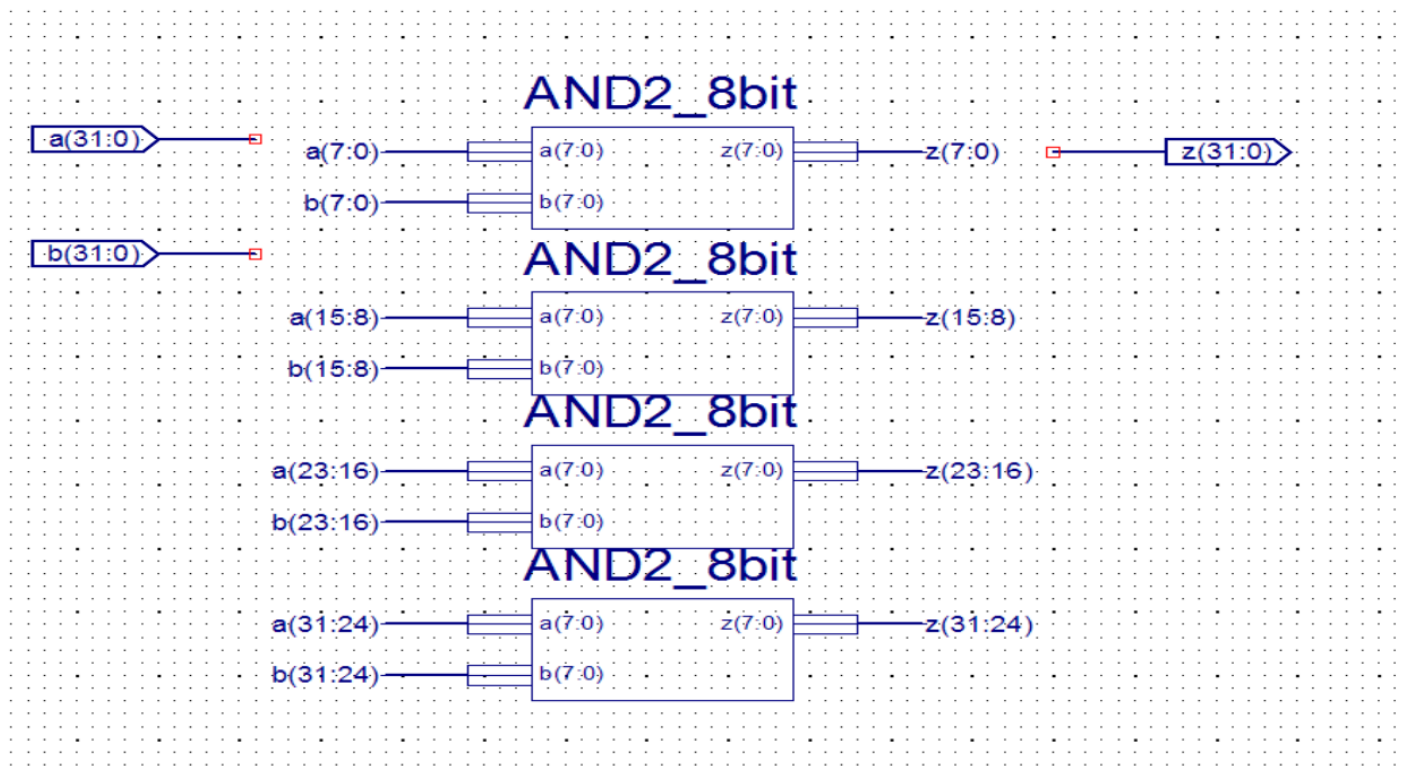


Figure 14: 32-bit and

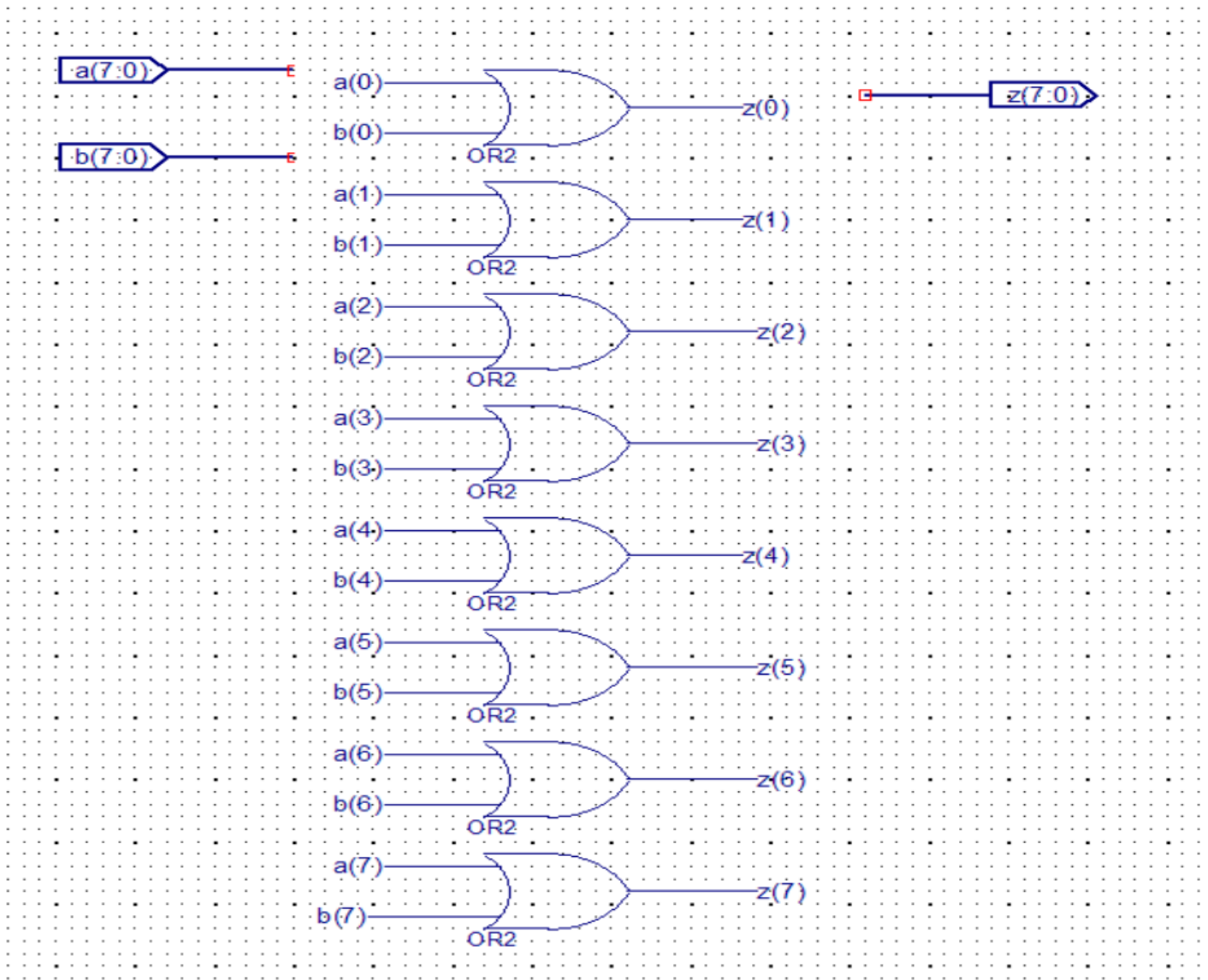


Figure 15: 8-bit or

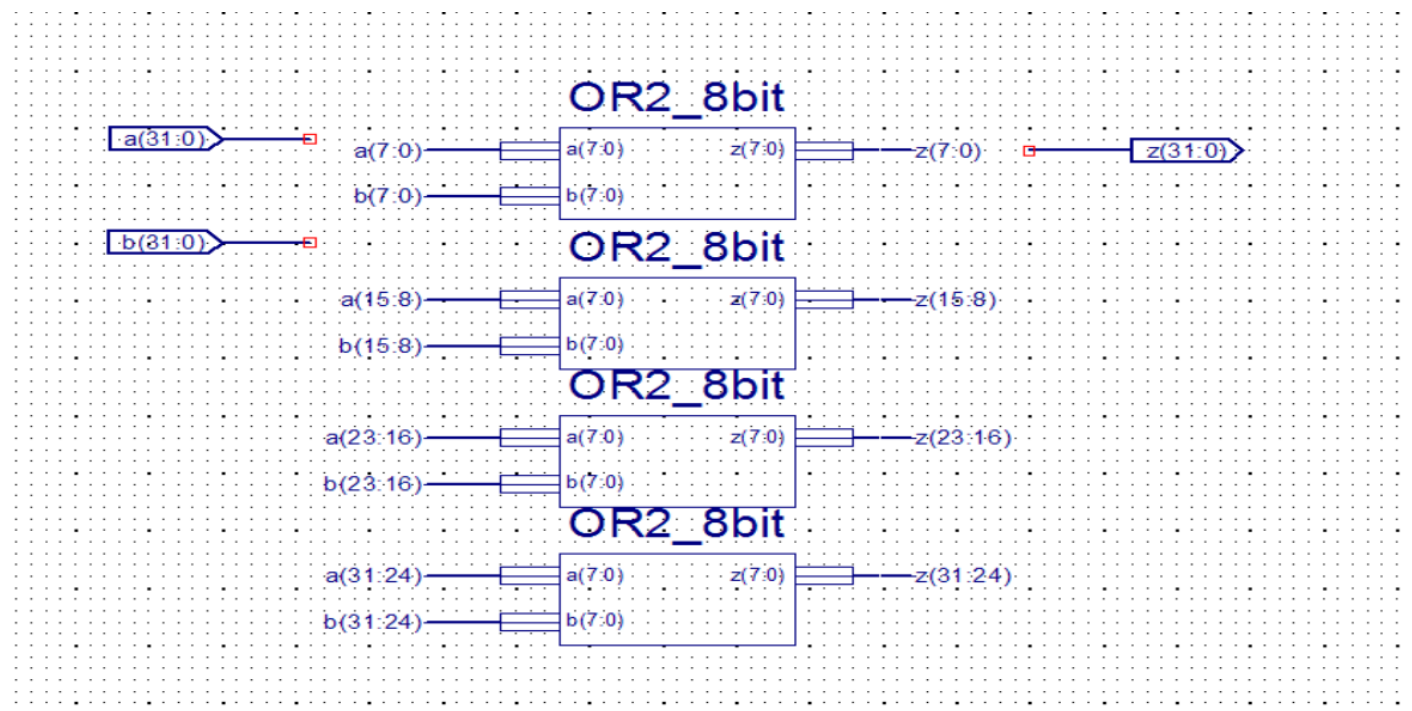


Figure 16: 32-bit or

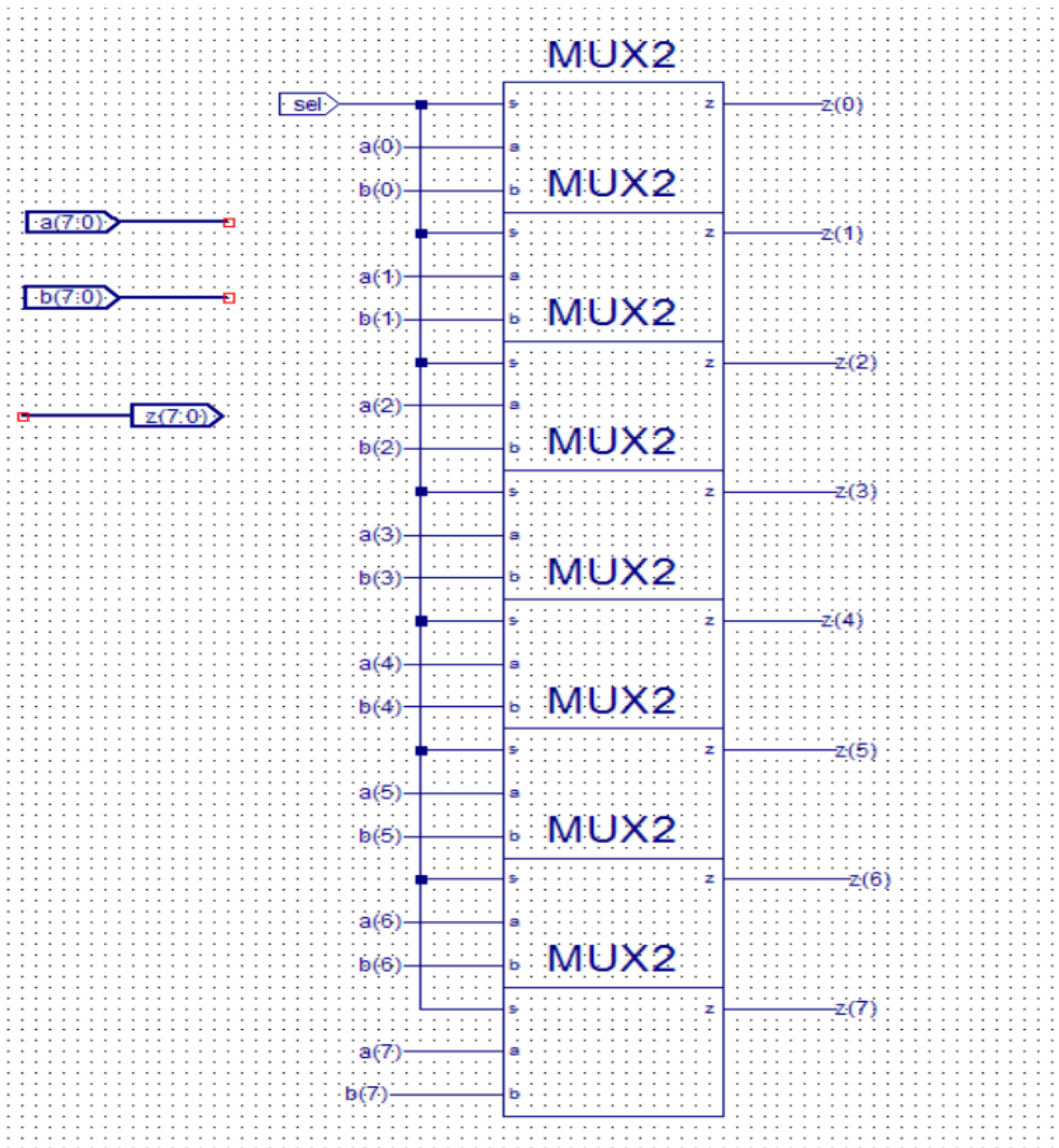


Figure 16: 8-bit 2-to-1 mux

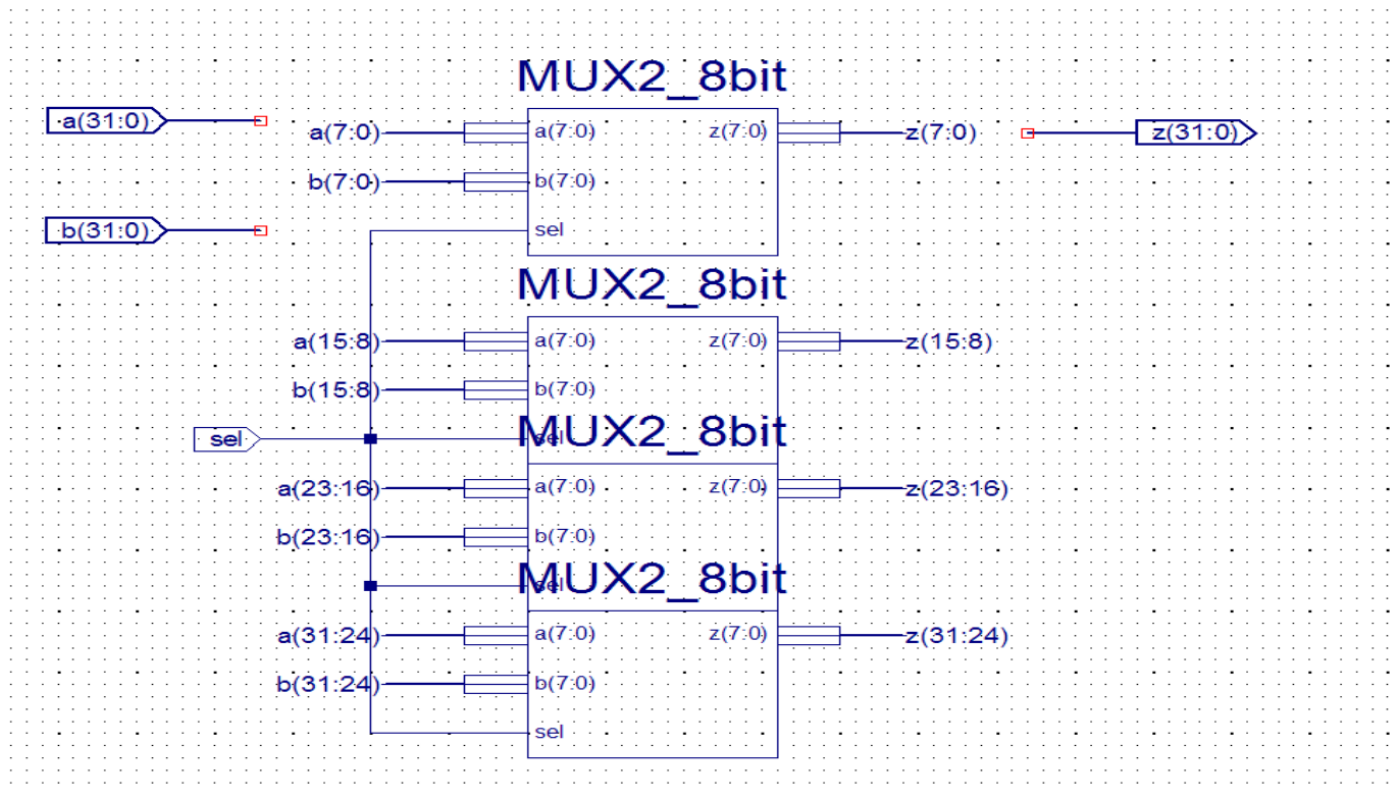


Figure 17: 32-bit 2-to-1 mux

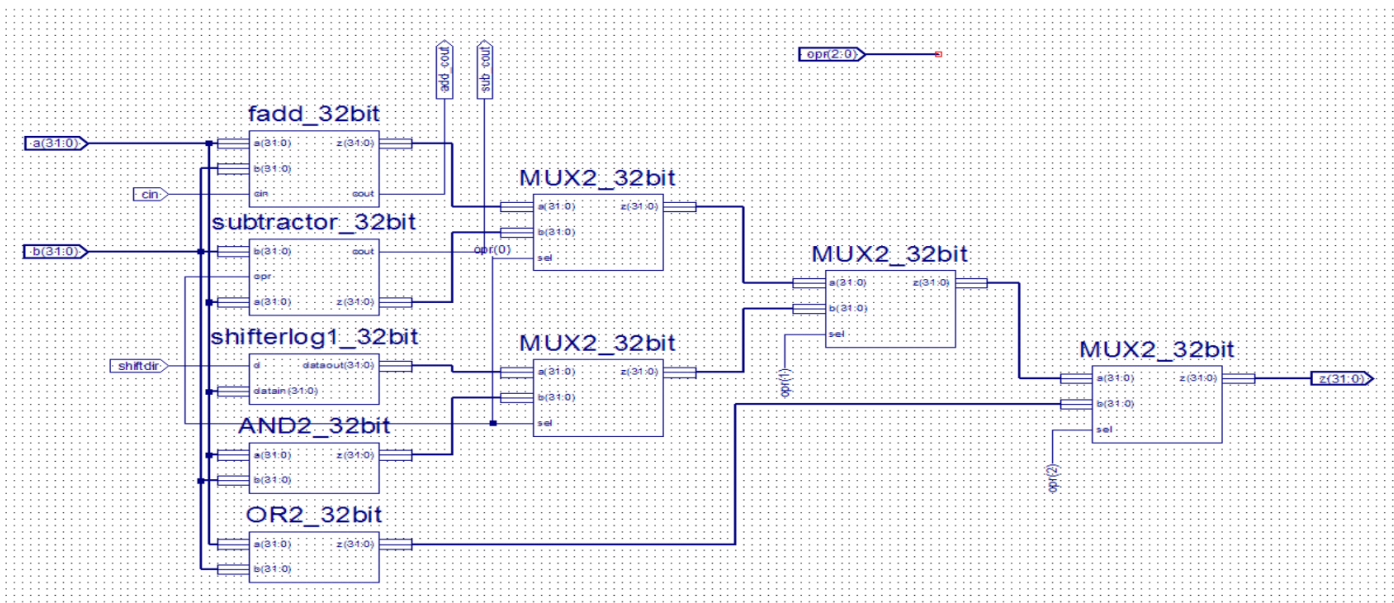


Figure 18: 32-bit ALU

 


Figure 19: waveform of 32-bit ALU (1)

 


Figure 20: waveform of 32-bit ALU (2)

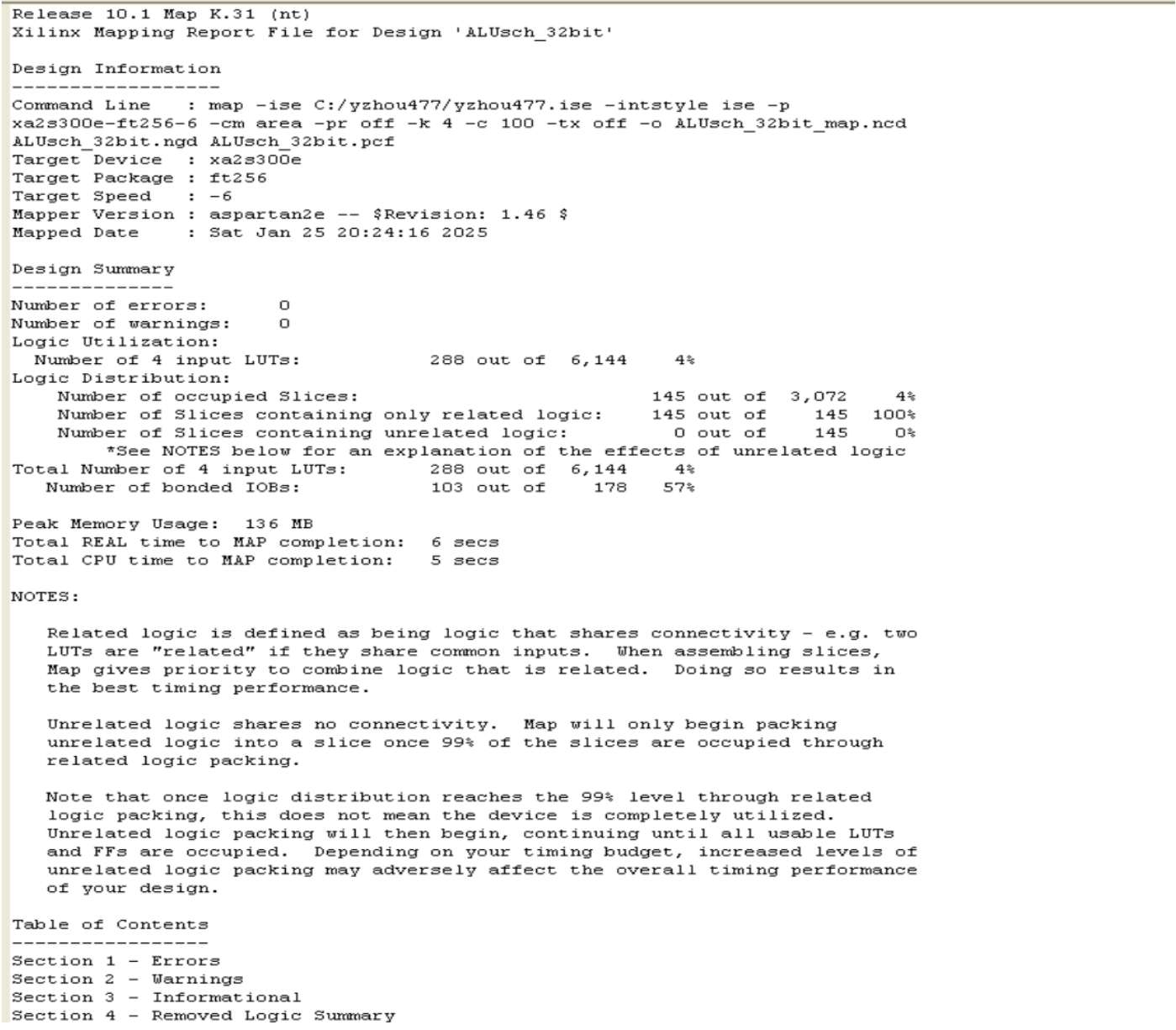


Figure 21: map report of 32-bit ALU

32-bit ALU Verilog:

 


Figure 22: waveform of 32-bit ALU verilog (1)

 


Figure 23: waveform of 32-bit ALU verilog (2)

```

Design Information
-----
Command Line   : map -ise C:/yzhou477/yzhou477.ise -intstyle ise -p
xa2s300e-ft256-6 -cm area -pr off -k 4 -c 100 -tx off -o ALUv_32bit_map.ncd
ALUv_32bit.ngd ALUv_32bit.pcf
Target Device  : xa2s300e
Target Package : ft256
Target Speed   : -6
Mapper Version : aspartan2e -- $Revision: 1.46 $
Mapped Date    : Sat Jan 25 20:53:03 2025

Design Summary
-----
Number of errors:      0
Number of warnings:    1
Logic Utilization:
  Number of 4 input LUTs:      194 out of  6,144    3%
Logic Distribution:
  Number of occupied Slices:    99 out of  3,072    3%
  Number of Slices containing only related logic:  99 out of    99 100%
  Number of Slices containing unrelated logic:      0 out of    99   0%
    *See NOTES below for an explanation of the effects of unrelated logic
Total Number of 4 input LUTs:  194 out of  6,144    3%
  Number of bonded IOBs:      102 out of   178   57%

Peak Memory Usage:  135 MB
Total REAL time to MAP completion:  8 secs
Total CPU time to MAP completion:    6 secs

NOTES:

  Related logic is defined as being logic that shares connectivity - e.g. two
  LUTs are "related" if they share common inputs.  When assembling slices,
  Map gives priority to combine logic that is related.  Doing so results in
  the best timing performance.

  Unrelated logic shares no connectivity.  Map will only begin packing
  unrelated logic into a slice once 99% of the slices are occupied through
  related logic packing.

  Note that once logic distribution reaches the 99% level through related
  logic packing, this does not mean the device is completely utilized.
  Unrelated logic packing will then begin, continuing until all usable LUTs
  and FFs are occupied.  Depending on your timing budget, increased levels of
  unrelated logic packing may adversely affect the overall timing performance
  of your design.

Table of Contents
-----
Section 1 - Errors
Section 2 - Warnings
Section 3 - Informational
Section 4 - Removed Logic Summary
Section 5 - Removed Logic
Section 6 - IOB Properties
Section 7 - RPMs
Section 8 - Guide Report

```

Figure 24: map report of 32-bit ALU Verilog

Comment:

In my design, Verilog gates (194) are much less than schematic gates (288). This means there is some logical redundancy in my schematic design.